

# ECS 203 (ME2) - Part 3A

## Dr.Prapun Sukksompong

### CHAPTER 9

#### Sinusoids and Phasors

We now begins the analysis of circuits in which the voltage or current sources are time-varying. In this chapter, we are particularly interested in sinusoidally time-varying excitation, or simply, excitation by a sinusoid.

9.0.1. Some terminology:

- (a) A **sinusoid** is a signal that has the form of the sine or cosine function.
  - Turn out that you can express them all under the same notation using only cosine (or only sine) function. We ill use cosine.
- (b) A sinusoidal current is referred to as **alternating current (AC)**.
- (c) Circuits driven by sinusoidal current or voltage sources are called **AC circuits**.

#### 9.1. Sinusoids

9.1.1. Consider the sinusoidal signal (in cosine form)

$$x(t) = X_m \cos(\omega t + \phi) = X_m \cos(2\pi f t + \phi),$$

where

- $X_m$ : the amplitude of the sinusoid,
- $\omega$ : the angular frequency in radians/s (or rad/s),
- $\phi$ : the phase.
  - First, we consider the case when  $\phi = 0$ :

- When  $\phi \neq 0$ , we shift the graph of  $X_m \cos(\omega t)$  to the **left** “by  $\phi$ ”.

9.1.2. The **period** (the time of one complete cycle) of the sinusoid is

$$T = \frac{2\pi}{\omega}.$$

The unit of the period is in second if the angular frequency unit is in radian per second.

The **frequency**  $f$  (the number of cycles per second or hertz (Hz)) is the reciprocal of this quantity, i.e.,

$$f = \frac{1}{T}.$$

9.1.3. **Standard form** for sinusoid: In this class, when you are asked to find the sinusoid representation of a signal, make sure that your answer is in the form

$$x(t) = X_m \cos(\omega t + \phi) = X_m \cos(2\pi f t + \phi),$$

where  $X_m$  is nonnegative and  $\phi$  is between  $-180^\circ$  and  $+180^\circ$ .

- When the signal is given in the sine form, it can be converted into its cosine form via the identity

$$\sin(x) = \cos(x - 90^\circ).$$

In particular,

$$X_m \sin(\omega t + \phi) = X_m \cos(\omega t + \phi - 90^\circ).$$

- $X_m$  is always non-negative. We can avoid having the negative sign by the following conversion:

$$-\cos(x) = \cos(x \pm 180^\circ).$$

In particular,

$$-A \cos(\omega t + \phi) = A \cos(2\pi f t + \phi \pm 180^\circ).$$

Note that usually you do not have the choice between  $+180^\circ$  or  $-180^\circ$ . The one that you need to use is the one that makes  $\phi \pm 180^\circ$  falls somewhere between  $-180^\circ$  and  $+180^\circ$ .

## 9.2. Phasors

Sinusoids are easily expressed in terms of phasors, which are more convenient to work with than sine and cosine functions. The tradoff is that phasors are complex-valued.

9.2.1. The idea of phasor representation is based on Euler's identity:

$$e^{j\phi} = \cos \phi + j \sin \phi,$$

From the identity, we may regard  $\cos \phi$  and  $\sin \phi$  as the real and imaginary parts of  $e^{j\phi}$ :

$$\cos \phi = \operatorname{Re} \{e^{j\phi}\}, \quad \sin \phi = \operatorname{Im} \{e^{j\phi}\},$$

where  $\operatorname{Re}$  and  $\operatorname{Im}$  stand for the real part of and the imaginary part of  $e^{j\phi}$ .

9.2.2. A phasor is a complex number that represents the amplitude and phase of a sinusoid. Given a sinusoid  $v(t) = V_m \cos(\omega t + \phi)$ , then

$$v(t) = V_m \cos(\omega t + \phi) = \operatorname{Re} \{V_m e^{j(\omega t + \phi)}\} = \operatorname{Re} \{V_m e^{j\phi} \cdot e^{j\omega t}\} = \operatorname{Re} \{\mathbf{V} e^{j\omega t}\},$$

where

$$\mathbf{V} = V_m e^{j\phi} = V_m \angle \phi.$$

$\mathbf{V}$  is called the **phasor representation** of the sinusoid  $v(t)$ . In other words, a phasor is a complex number that represents amplitude and phase of a sinusoid.

9.2.3. Remarks:

- Whenever a sinusoid is expressed as a phasor, the term  $e^{j\omega t}$  is **implicitly** present. It is therefore important, when dealing with phasors, to keep in mind the (angular) frequency  $\omega$  of the phasor.

- To obtain the sinusoid corresponding to a given phasor  $\mathbf{V}$ , multiply the phasor by the time factor  $e^{j\omega t}$  and take the real part.

Equivalently, given a phasor, we obtain the time-domain representation as the cosine function with the same magnitude as the phasor and the argument as  $\omega t$  plus the phase of the phasor.

- Any complex number  $z$  (including any phasor) can be equivalently represented in three forms.

(a) Rectangular form:  $z = x + jy$ .

(b) Polar form:  $z = r\angle\phi$ .

(c) Exponential form:  $z = re^{j\phi}$

where the relations between them are

$$r = \sqrt{x^2 + y^2}, \quad \phi = \tan^{-1} \frac{y}{x} \pm 180^\circ.$$

$$x = r \cos \phi, \quad y = r \sin \phi.$$

Note that for  $\phi$ , the choice of using  $+180^\circ$  or  $-180^\circ$  in the formula is determined by the actual quadrant in which the complex number lies.

- As a complex quantity, a phasor may be expressed in rectangular form, polar form, or exponential form. In this class, we focus on polar form.

**9.2.4. Summary:** By suppressing the time factor, we transform the sinusoid from the time domain to the phasor domain. This transformation is summarized as follows:

$$v(t) = V_m \cos(\omega t + \phi) \Leftrightarrow \mathbf{V} = V_m \angle \phi.$$

Time domain representation  $\Leftrightarrow$  Phasor domain representation

9.2.5. **Standard form** for phasor: In this class, when you are asked to find the phasor representation of a signal, make sure that your answer is a complex number in polar form, i.e.  $r\angle\phi$  where  $r$  is nonnegative and  $\phi$  is between  $-180^\circ$  and  $+180^\circ$ .

EXAMPLE 9.2.6. Transform these sinusoids to phasors:

(a)  $i = 6 \cos(50t - 40^\circ)$  A

(b)  $v = -4 \sin(30t + 50^\circ)$  V

EXAMPLE 9.2.7. Find the sinusoids represented by these phasors:

(a)  $\mathbf{I} = -3 + j4$  A

(b)  $\mathbf{V} = j8e^{-j20^\circ}$  V

9.2.8. The differences between  $v(t)$  and  $\mathbf{V}$  should be emphasized:

- (a)  $v(t)$  is the instantaneous or time-domain representation, while  $V$  is the frequency or phasor-domain representation.
- (b)  $v(t)$  is time dependent, while  $\mathbf{V}$  is not.
- (c)  $v(t)$  is always real with no complex term, while  $\mathbf{V}$  is generally complex.

9.2.9. Adding sinusoids of the *same frequency* is equivalent to adding their corresponding phasors. To see this,

$$\begin{aligned} A_1 \cos(\omega t + \phi_1) + A_2 \cos(\omega t + \phi_2) &= \operatorname{Re} \{ \mathbf{A}_1 e^{j\omega t} \} + \operatorname{Re} \{ \mathbf{A}_2 e^{j\omega t} \} \\ &= \operatorname{Re} \{ (\mathbf{A}_1 + \mathbf{A}_2) e^{j\omega t} \}. \end{aligned}$$

9.2.10. Properties involving differentiation and integration:

- (a) **Differentiating** a sinusoid is equivalent to multiplying its corresponding phasor by  $j\omega$ . In other words,

$$\frac{dv(t)}{dt} \Leftrightarrow j\omega \mathbf{V}.$$

To see this, suppose  $v(t) = V_m \cos(\omega t + \phi)$ . Then,

$$\begin{aligned} \frac{dv}{dt}(t) &= -\omega V_m \sin(\omega t + \phi) = \omega V_m \cos(\omega t + \phi - 90^\circ + 180^\circ) \\ &= \operatorname{Re} \{ \omega V_m e^{j\phi} e^{j90^\circ} \cdot e^{j\omega t} \} = \operatorname{Re} \{ j\omega \mathbf{V} e^{j\omega t} \} \end{aligned}$$

Alternatively, express  $v(t)$  as

$$v(t) = \operatorname{Re} \left\{ V_m e^{j(\omega t + \phi)} \right\}.$$

Then,

$$\frac{d}{dt}v(t) = \operatorname{Re} \left\{ V_m j\omega e^{j(\omega t + \phi)} \right\}.$$

- (b) **Integrating** a sinusoid is equivalent to dividing its corresponding phasor by  $j\omega$ . In other words,

$$\int v(t) dt \Leftrightarrow \frac{\mathbf{V}}{j\omega}.$$

EXAMPLE 9.2.11. Find the voltage  $v(t)$  in a circuit described by the integrodifferential equation

$$2 \frac{dv}{dt} + 5v + 10 \int v dt = 20 \cos(5t - 30^\circ)$$

using the phasor approach.


### 9.3. Phasor relationships for circuit elements

9.3.1. Resistor  $R$ : If the current through a resistor  $R$  is

$$i(t) = I_m \cos(\omega t + \phi) \Leftrightarrow \mathbf{I} = I_m \angle \phi,$$

the voltage across it is given by
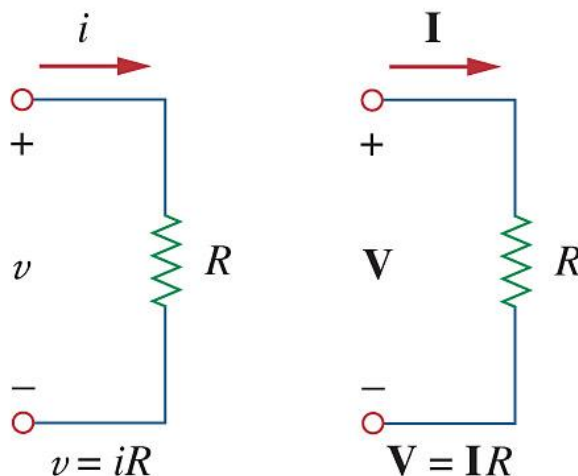
$$v(t) = i(t)R = RI_m \cos(\omega t + \phi).$$




The phasor of the voltage is

$$\mathbf{V} = RI_m \angle \phi.$$

Hence,

$$\mathbf{V} = \mathbf{I}R.$$

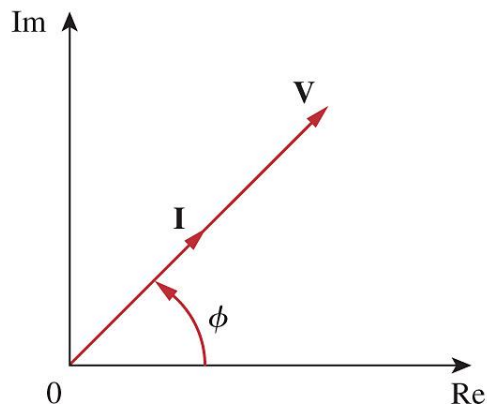We note that voltage and current are **in phase** and that the voltage-current relation for the resistor in the phasor domain continues to be Ohms law, as in the time domain.




9.3.2. Capacitor  $C$ : If the voltage across a capacitor  $C$  is


$$v(t) = V_m \cos(\omega t + \phi) \Leftrightarrow \mathbf{V} = V_m \angle \phi,$$

the current through it is given by
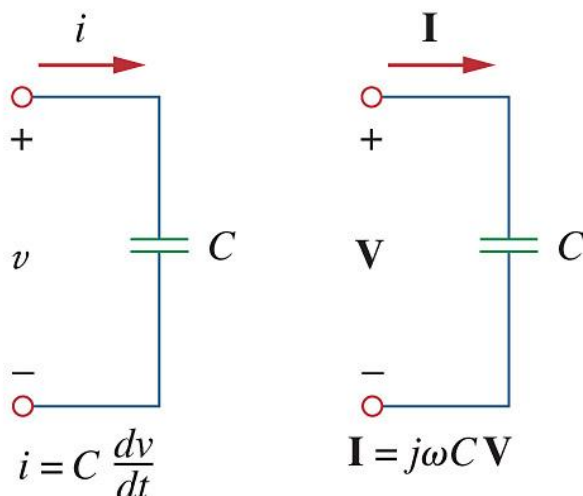
$$i(t) = C \frac{dv(t)}{dt} \Leftrightarrow \mathbf{I} = j\omega C \mathbf{V} = \omega C V_m \angle (\phi + 90^\circ).$$



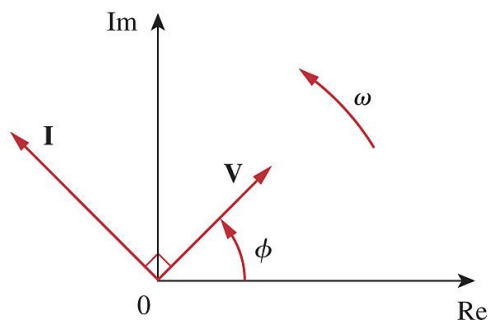The voltage and current are  $90^\circ$  out of phase. Specifically, the current leads the voltage by  $90^\circ$ .



- Mnemonic: CIVIL

In a Capacitive (C) circuit, I leads V. In an inductive (L) circuit, V leads V.




9.3.3. Inductor  $L$ : If the current through an inductor  $L$  is


$$i(t) = I_m \cos(\omega t + \phi) \Leftrightarrow \mathbf{I} = I_m \angle \phi,$$

the voltage across it is given by
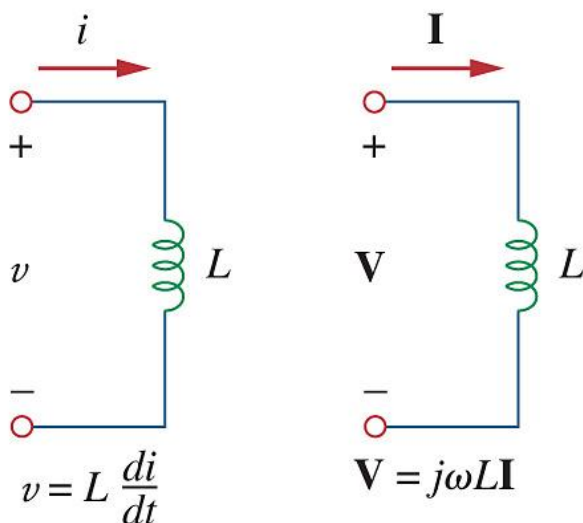
$$v(t) = L \frac{di(t)}{dt} \Leftrightarrow \mathbf{V} = j\omega L \mathbf{I} = \omega L I_m \angle (\phi + 90^\circ).$$



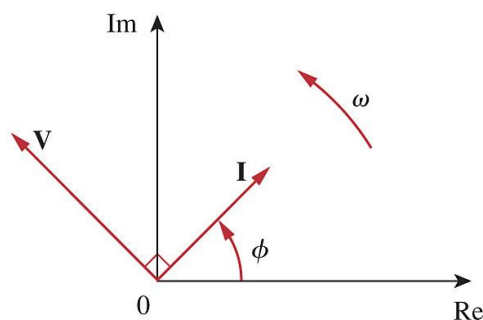The voltage and current are  $90^\circ$  out of phase. Specifically, the current lags the voltage by  $90^\circ$ .



Element	Time domain	Frequency domain
$R$	$v = Ri$	$\mathbf{V} = R\mathbf{I}$
$L$	$v = L \frac{di}{dt}$	$\mathbf{V} = j\omega L \mathbf{I}$
$C$	$i = C \frac{dv}{dt}$	$\mathbf{V} = \frac{\mathbf{I}}{j\omega C}$

### 9.4. Impedance and Admittance

Thus, we obtained the voltage current relations for the three passive elements as

$$\mathbf{V} = \mathbf{I}R, \quad \mathbf{V} = j\omega L\mathbf{I}, \quad \mathbf{I} = j\omega C\mathbf{V}.$$

These equations may be written in terms of the ratio of the phasor voltage to the phasor of current as

$$\frac{\mathbf{V}}{\mathbf{I}} = R, \quad \frac{\mathbf{V}}{\mathbf{I}} = j\omega L, \quad \frac{\mathbf{V}}{\mathbf{I}} = \frac{1}{j\omega C}.$$

From these equations, we obtain Ohm's law in phasor form for any type of element as

$$\mathbf{Z} = \frac{\mathbf{V}}{\mathbf{I}} \quad \text{or} \quad \mathbf{V} = \mathbf{I}\mathbf{Z}.$$

**DEFINITION 9.4.1.** The impedance  $\mathbf{Z}$  of a circuit is the ratio of the phasor voltage  $\mathbf{V}$  to the phasor current  $\mathbf{I}$ , measured in ohms ( $\Omega$ ).

As a complex quantity, the impedance may be expressed in rectangular form as

$$\mathbf{Z} = R + jX = |\mathbf{Z}|\angle\theta,$$

with

$$|\mathbf{Z}| = \sqrt{R^2 + X^2}, \quad \theta = \tan^{-1} \frac{X}{R}, \quad R = |\mathbf{Z}| \cos \theta, \quad X = |\mathbf{Z}| \sin \theta.$$

$R = \text{Re}\{\mathbf{Z}\}$  is called the **resistance** and  $X = \text{Im}\{\mathbf{Z}\}$  is called the **reactance**.

The reactance  $X$  may be positive or negative. We say that the impedance is **inductive** when  $X$  is positive or **capacitive** when  $X$  is negative.

**DEFINITION 9.4.2.** The **admittance** ( $\mathbf{Y}$ ) is the reciprocal of impedance, measured in Siemens (S). The admittance of an element (or a circuit) is the ratio of the phasor current through it to phasor voltage across it, or

$$\mathbf{Y} = \frac{1}{\mathbf{Z}} = \frac{\mathbf{I}}{\mathbf{V}}.$$

### 9.4.3. Kirchhoff's laws (KCL and KVL) hold in the phasor form.

To see this, suppose  $v_1, v_2, \dots, v_n$  are the voltages around a closed loop, then

$$v_1 + v_2 + \dots + v_n = 0.$$

If each voltage  $v_i$  is a sinusoid, i.e.

$$v_i = V_{mi} \cos(\omega t + \phi_i) = \operatorname{Re} \{ \mathbf{V}_i e^{j\omega t} \}$$

with phasor  $\mathbf{V}_i = V_{mi} \angle \phi_i = V_{mi} e^{j\phi_i}$ , then

$$\operatorname{Re} \{ (\mathbf{V}_1 + \mathbf{V}_2 + \dots + \mathbf{V}_n) e^{j\omega t} \} = 0,$$

which must be true for all time  $t$ . To satisfy this, we need

$$\mathbf{V}_1 + \mathbf{V}_2 + \dots + \mathbf{V}_n = 0.$$

Hence, KVL holds for phasors.

Similarly, we can show that KCL holds in the frequency domain, i.e., if the currents  $i_1, i_2, \dots, i_n$  be the currents entering or leaving a closed surface at time  $t$ , then

$$i_1 + i_2 + \dots + i_n = 0.$$

If the currents are sinusoids and  $\mathbf{I}_1, \mathbf{I}_2, \dots, \mathbf{I}_n$  are their phasor forms, then

$$\mathbf{I}_1 + \mathbf{I}_2 + \dots + \mathbf{I}_n = 0.$$


**Major Implication:** Since Ohm's Law and Kirchhoff's Laws hold in phasor domain, **all resistance combination, analysis methods** (nodal and mesh analysis) **and circuit theorems** (linearity, superposition, source transformation, and Thevenin's and Norton's equivalent circuits) that we have previously studied for dc circuits **apply to ac circuits!!!**

**Just think of impedance as a complex-valued resistance!!**

In addition, our ac circuits can now effortlessly include capacitors and inductors which can be considered as impedances whose values depend on the frequency  $\omega$  of the ac sources!!
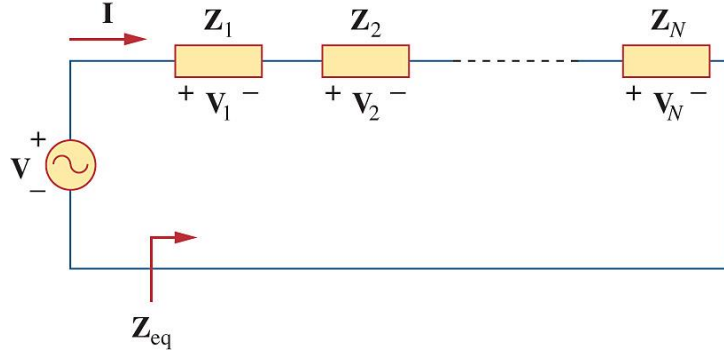
### 9.5. Impedance Combinations

Consider  $N$  series-connected impedances as shown below.




The same current  $I$  flows through the impedances. Applying KVL around the loop gives

$$V = V_1 + V_2 + \cdots + V_N = I(Z_1 + Z_2 + \cdots + Z_N)$$

The equivalent impedance at the input terminals is

$$Z_{eq} = \frac{V}{I} = Z_1 + Z_2 + \cdots + Z_N.$$

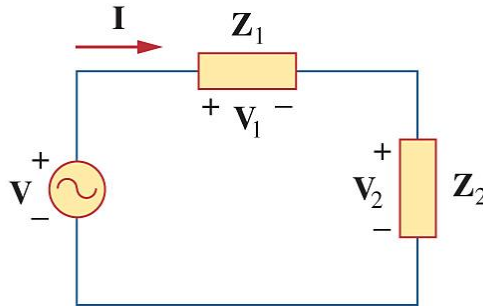In particular, if  $N = 2$ , the current through the impedance is




$$I = \frac{V}{Z_1 + Z_2}.$$

Because  $V_1 = Z_1 I$  and  $V_2 = Z_2 I$ ,

$$V_1 = \frac{Z_1}{Z_1 + Z_2} V, \quad V_2 = \frac{Z_2}{Z_1 + Z_2} V$$

which is the **voltage-division** relationship.

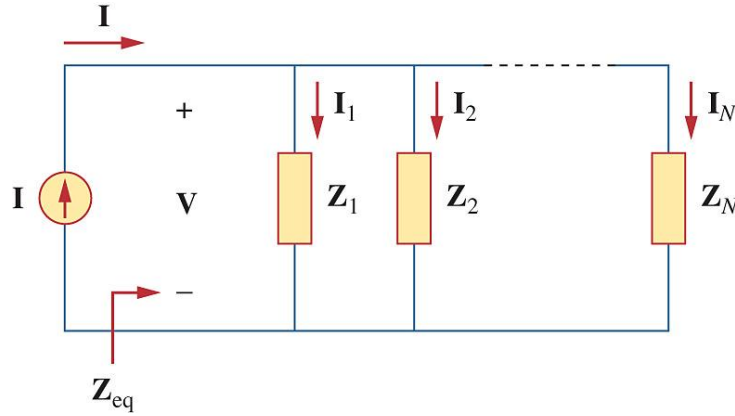Now, consider  $N$  parallel-connected impedances as shown below.



The voltage across each impedance is the same. Applying KCL at the top node gives

$$I = I_1 + I_2 + \dots + I_N = V \left( \frac{1}{Z_1} + \frac{1}{Z_2} + \dots + \frac{1}{Z_N} \right).$$

The equivalent impedance  $Z_{eq}$  can be found from

$$\frac{1}{Z_{eq}} = \frac{I}{V} = \frac{1}{Z_1} + \frac{1}{Z_2} + \dots + \frac{1}{Z_N}.$$

When  $N = 2$ ,

$$Z_{eq} = \frac{Z_1 Z_2}{Z_1 + Z_2}.$$


Because

$$V = I Z_{eq} = I_1 Z_1 = I_2 Z_2,$$


we have

$$I_1 = \frac{Z_2}{Z_1 + Z_2} I, \quad I_2 = \frac{Z_1}{Z_1 + Z_2} I$$

which is the **current-division** principle.

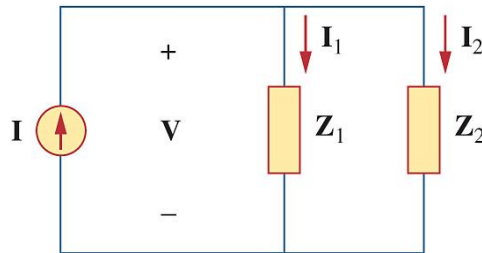

EXAMPLE 9.5.1. Find the input impedance of the circuit below. Assume that the circuit operates at  $\omega = 50$  rad/s.

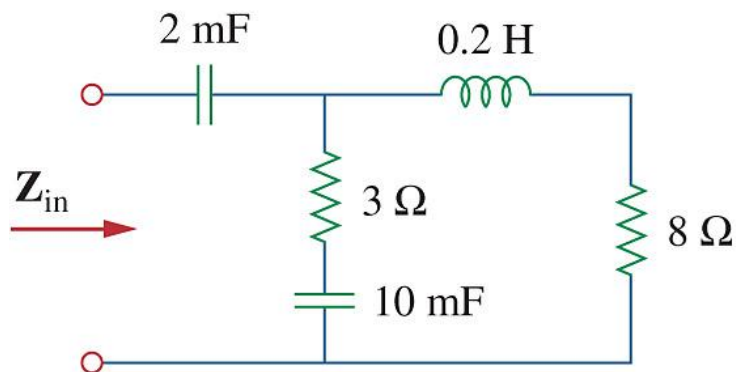

EXAMPLE 9.5.2. Determine  $v_o(t)$  in the circuit below.

