

$$i_1 + i_2 = i_3 \quad \text{--- (1)}$$

$$\frac{Vi - V_A}{R_1} + \frac{V_A}{R_i} = \frac{V_A - V_B}{R_f} \quad \text{--- (2)}$$

$$\text{from (2) } V_A = 0 \quad \text{--- (3)}$$

from (3) into (2)

$$\frac{Vi}{R_1} = -\frac{V_B}{R_f} \quad \text{--- (4)}$$

$$V_B = V_0 \quad \text{--- (5)}$$

from (5) into (4)

$$\frac{Vi}{R_1} = -\frac{V_0}{R_f}$$


Inverting Amplifier


$$\frac{V_0}{Vi} = -\frac{R_f}{R_1}$$

$$V_0 = -\frac{R_f}{R_1} Vi$$


$$-5V = V_0 = -A_{in} Vi$$

Invert (180°)

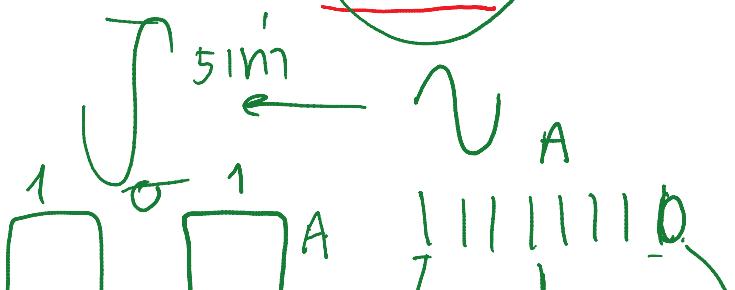

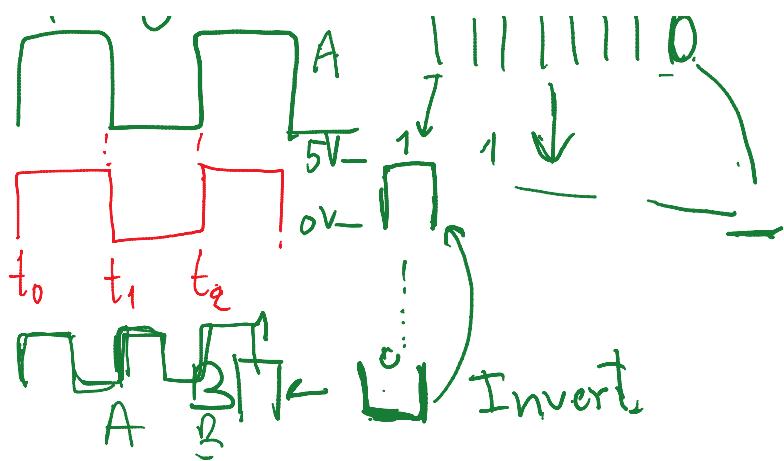

Non-Inverting Amplifier

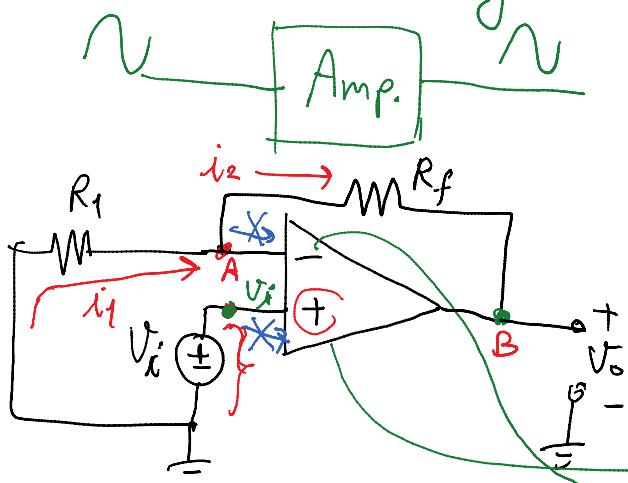

① กฎของกราดอนเดอร์ $V_A = V_i$ ดังนั้น $V_- = V_+$

② ใช้เข็มไฟ A กฎ KCL

$$i_1 = i_2 \quad \text{---} \quad ①$$

$$\frac{V_A - V_-}{R_1} = \frac{V_A - V_o}{R_f} \quad \text{---} \quad ②$$

$$\text{ดังนั้น } V_A = V_i \quad \text{---} \quad ③$$


ดังนั้น ③ นำมายัง ②

$$\frac{-V_i}{R_1} = \frac{V_i - V_o}{R_f} \quad \text{---} \quad ④$$

$$-V_i \left(\frac{1}{R_1} + \frac{1}{R_f} \right) = -V_o \quad \text{---} \quad ⑤$$

$$\frac{V_o}{V_i} = 1 + \frac{R_f}{R_1} \quad \text{***}$$

Voltage follower (Buffer)

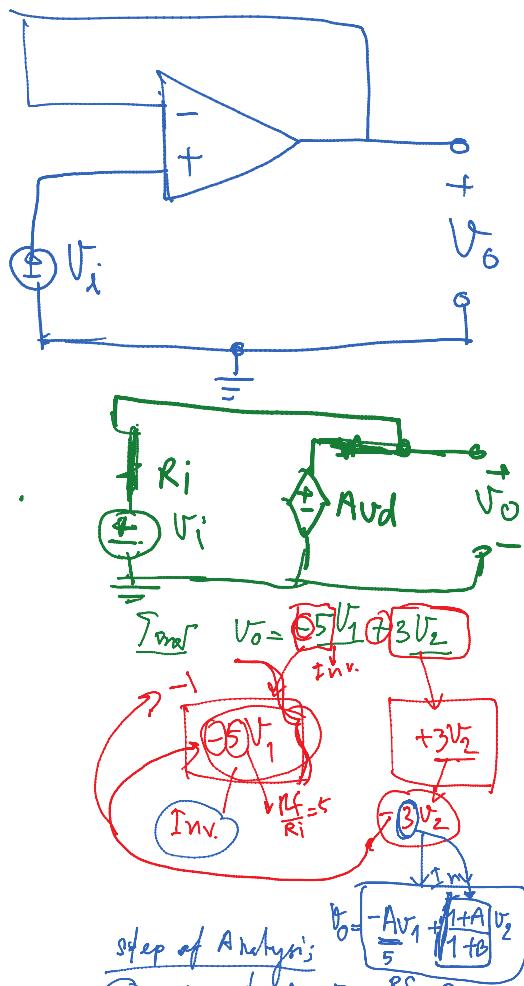

$$\text{Step of A analysis: } V_o = \frac{-A V_1 + (1+A) V_2}{1+B}$$

1 We set $A = 5 \Rightarrow \frac{R_f}{R_1} = 5$
 2 Minus $R_2 = R_f = 5 \Rightarrow R_2 = 5 R_1$
 3 Minus $R_1 = 10 k\Omega \Rightarrow R_2 = 50 k\Omega$
 4 Minus $3 = \frac{1+A}{1+B} \Rightarrow 3 = \frac{1+5}{1+B}$

$$3(1+B) = 1+5$$


$$1+B = 2$$






$$B = 1 \quad \times$$

$$\text{in difference Amp we } B = \frac{R_2}{R_4}$$


$$\frac{R_2}{R_4} = 1 \Rightarrow R_2 = R_4$$
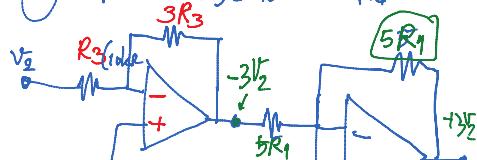
$$5 \quad \text{Minus } R_3 = 10 k\Omega = R_4$$



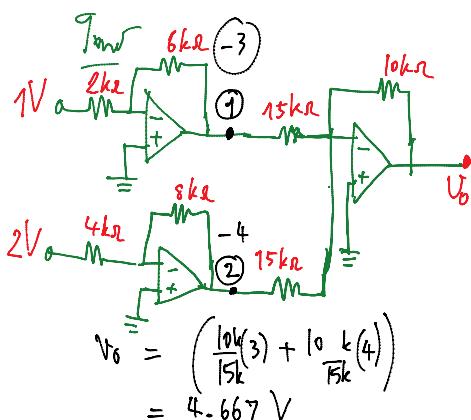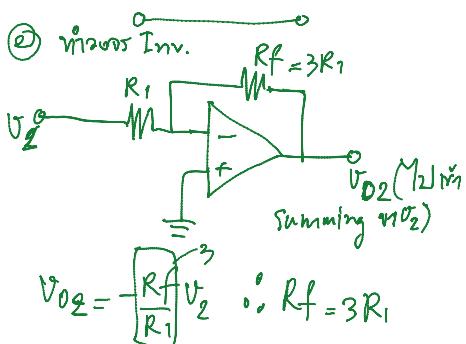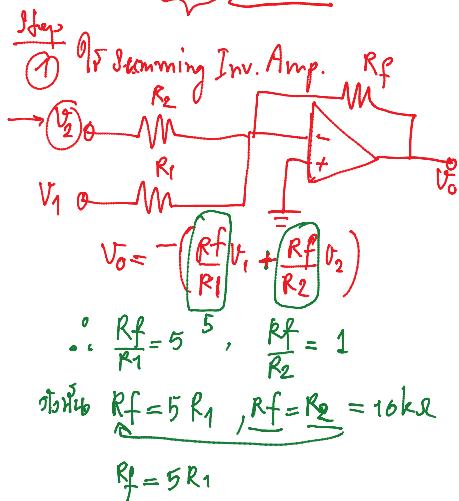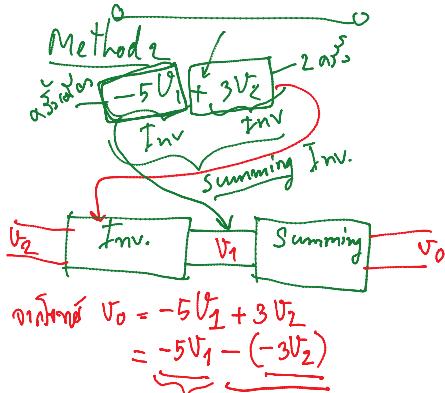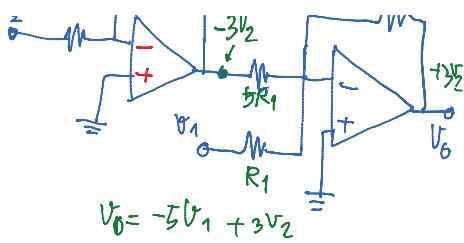

~~- Ideal case~~
~~- non-Ideal case~~

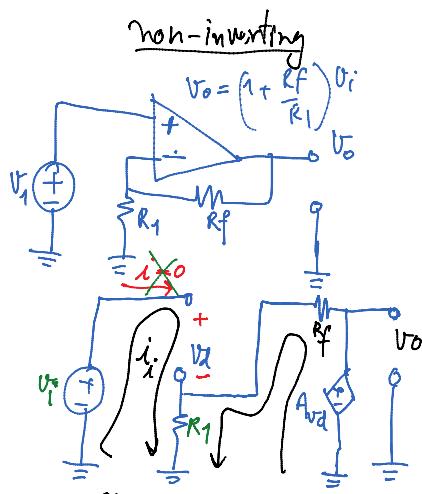

Mesh (ii)

$$-V_i + V_d + i_f R_1 + i_f R_f = 0 \quad (1)$$

then since $i_f = 0 \therefore$

$$-V_i + V_d + i_f R_1 = 0 \quad (2)$$

Mesh (if)

$$\text{then } A_{vd} = V_o$$

$$-V_o + i_f R_f + i_f R_1 + i_f R_1 = 0 \quad (3)$$

$$V_o = i_f (R_1 + R_f) \quad (4)$$

then (2) \approx (4) \therefore

$$\text{if } R_1 = V_i - V_d$$

$$\therefore i_f = \frac{V_i - V_d}{R_1} \quad (5)$$

then (3) \approx (5)

$$V_o = \left(\frac{V_i - V_d}{R_1} \right) (R_1 + R_f) \quad (6)$$

$$V_o = \frac{V_i (R_1 + R_f)}{R_1} - \frac{V_d (R_1 + R_f)}{R_1} \quad (7)$$

then $A_{vd} = V_o$

$$\therefore V_d = \frac{V_o}{A} \quad (8)$$

then (8) minus (7)

$$V_o = \frac{V_i (R_1 + R_f)}{R_1} - \frac{V_o ((R_f + R_1))}{A \xrightarrow{R_1}} \quad (9)$$

$$V_o \left(1 + \frac{R_1 + R_f}{A R_1} \right) = V_i \left(\frac{R_1 + R_f}{R_1} \right) \quad (10)$$

$$(11) \therefore \frac{V_o}{V_i} = \frac{R_1 + R_f}{R_1} \left(1 + \frac{R_1 + R_f}{A R_1} \right)$$


$\therefore A = \text{non-inverting gain.}$

$$\boxed{\frac{V_o}{V_i} = \frac{R_1 + R_f}{R_1} \approx 1 + \frac{R_f}{R_1}}$$

- invert, non-invert, sum / buffer

$$A = \frac{dy}{dt} / \int y dt$$

Differentiator Amplifier

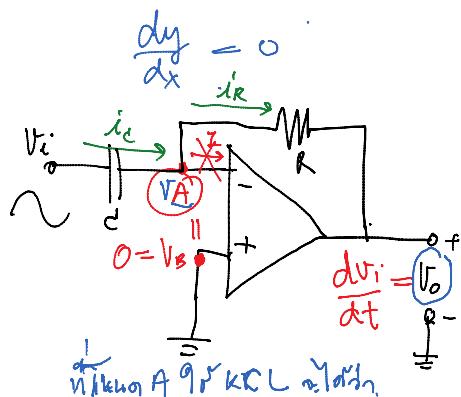

$$\frac{Vi - V_A}{C} = i_C = i_R \quad \text{--- (1)}$$

$$(Vi - V_A) \frac{dV_A}{dt} = V_A - V_o \quad \text{--- (2)}$$

$$(Vi - V_A) CS = \frac{V_A - V_o}{R} \quad \text{--- (3)}$$

then $V_A = 0$ result


$$V_i CS = -\frac{V_o}{R}$$

$$C \frac{dV_i}{dt} = -\frac{V_o}{R}$$

$$\frac{dV_i}{dt} = \frac{-V_o}{CR} \quad \text{A} \star \star$$

$$dV_i = -\frac{V_o}{CR} dt$$

Integrator Amplifier

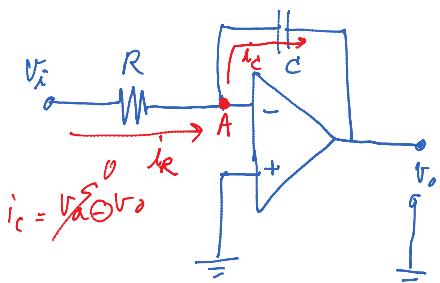


$$iR = iC$$


$$\frac{Vi - V_A}{R} = C \frac{dV_o}{dt}$$

$$\therefore V_o = \frac{-1}{Rc} \int V_i dt \quad \star \star$$
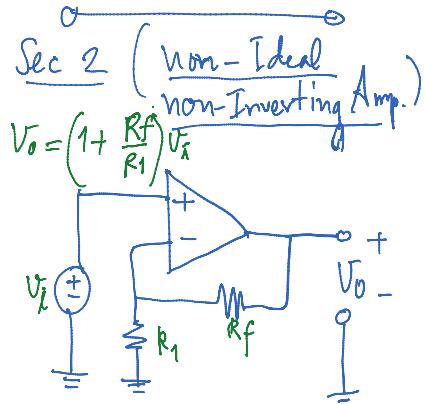
$$\therefore V_o = \frac{-1}{RC} \int V_i dt \quad \star\star$$



Now, $\frac{V_o}{V_i} = ?$

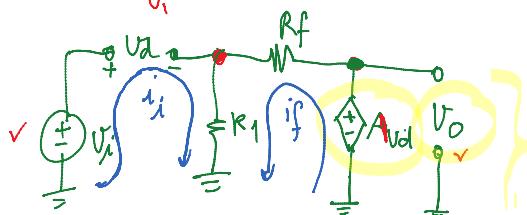

Mesh (ii)

$$-V_i + V_d + R_1(i_{ii} + i_{if}) = 0 \quad \textcircled{1}$$

$$-V_i + V_d + R_1 \cdot i_{if} = 0 \quad \textcircled{2}$$

Mesh (if)

$$-A V_d + i_{if} R_f + R_1(i_{if} + i_i) = 0 \quad \textcircled{3}$$

$$-AV_d + i_{if}(R_1 + R_f) = 0 \quad \textcircled{4}$$

$A V_d = V_o$

$$-V_o + i_{if}(R_1 + R_f) = 0 \quad \textcircled{5}$$

$$\therefore i_{if} = \frac{V_o}{R_1 + R_f} \quad \textcircled{6}$$

in (2) $i_{ii} - V_d = \frac{V_o}{A}$

$A V_d = V_o$

$$-V_i + \frac{V_o}{A} + R_1 i_{if} = 0 \quad \textcircled{7}$$

$$i_{if} = \left(V_i - \frac{V_o}{A} \right) \quad \textcircled{8}$$

$$\frac{V_o}{R_1 + R_f} = V_i - \frac{V_o}{A} \quad \textcircled{9}$$

$$\frac{V_o}{R_1 + R_f} = \frac{V_i - V_o}{R_1} \xrightarrow{\text{if}} \quad \textcircled{1}$$



$$V_o = V_i \frac{(R_f + R_1)}{R_1} - \frac{V_o}{A} \left(\frac{R_f + R_1}{R_1} \right) \quad \textcircled{2}$$

$$V_o \left(1 + \frac{R_f + R_1}{AR} \right) = V_i \left(\frac{R_f + R_1}{R_1} \right) \quad \textcircled{3}$$

$$\frac{V_o}{V_i} = \frac{R_f + R_1}{R_1} \Bigg/ \left(1 + \frac{R_f + R_1}{AR_1} \right)$$

$\text{In } A \gg (A= \text{open loop})$
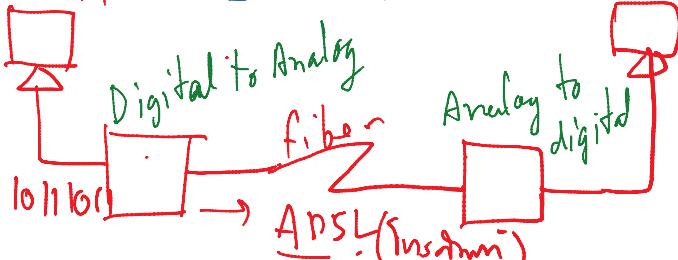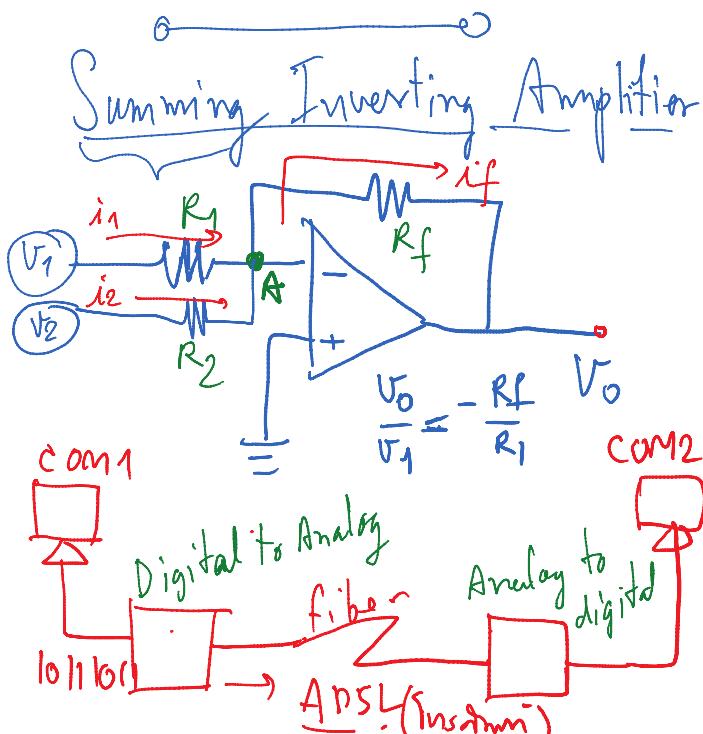
$$\therefore \frac{V_o}{V_i} = 1 + \frac{R_f}{R_1}$$



At node A $\sum KCL = 0$


$$i_1 + i_2 = if \xrightarrow{i_1 + i_2 = if} \quad \textcircled{1}$$

$$\frac{V_1 - 0}{R_1} + \frac{V_2 - 0}{R_2} = 0 - \frac{V_o}{R_f} \quad \textcircled{2}$$

$$V_o = - \left(\frac{V_1 \cdot R_f}{R_1} + \frac{V_2 \cdot R_f}{R_1} \right)$$

Internet: IFFT

Subtracting (difference) Amplifier

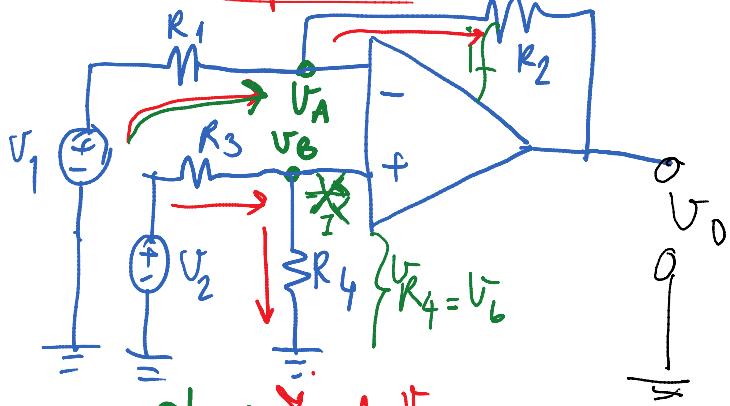

Step: Non-inverting node V_A

$$\text{Op-Amp Voltage Divider. } V_B = \frac{R_4 \cdot V_2}{R_3 + R_4} \quad \textcircled{1}$$

Non-inverting node V_B

$$\frac{V_2 - V_B}{R_3} = \frac{V_B - 0}{R_4} \quad \textcircled{2}$$

In \textcircled{1} and \textcircled{2}

$$\frac{V_2 - \left(\frac{R_4 \cdot V_2}{R_3 + R_4} \right)}{R_3} = \frac{\left(\frac{R_4 \cdot V_2}{R_3 + R_4} \right)}{R_4} \quad \textcircled{3}$$

$$\text{In } V_B = \frac{R_4 \cdot V_2}{R_3 + R_4} \rightarrow \text{in } R_4 \text{ will}$$

$$V_B = \frac{1}{\frac{R_3 + 1}{R_4}} V_2$$

$$\text{In } R_3/R_4 = B$$

$$V_B = \frac{1}{B+1} V_2 \quad \textcircled{4}$$

In \textcircled{4} and \textcircled{3}

$$\frac{V_2 - \left(\frac{V_2}{1+B} \right)}{R_3} = R_3 \left(\frac{V_2}{1+B} \right)$$

$$V_2 - \frac{V_2}{1+B} = \left[\frac{R_3}{R_4} \right] \left(\frac{V_2}{1+B} \right)$$

$$V_2 \left(1 - \frac{1}{1+B}\right) = \boxed{\frac{V_1}{R_1} \left(1 + \frac{1}{1+B}\right)}$$

$$V_2 \left(1 - \frac{1}{1+B}\right) = \frac{B}{1+B} V_2$$

At node V_A by KCL we get

if $\frac{V_1 - V_A}{R_1}$ is if $\frac{V_A - V_O}{R_L}$


$$V_A = V_A - i_f R_2$$

$$V_O = V_A - \frac{V_1 - V_A}{R_1} R_2 = A$$

$$V_O = V_A - (V_1 - V_A) A$$

$$V_O = -AV_1 + (1+A)V_A$$

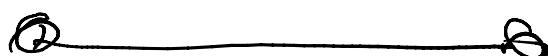
$$\boxed{V_O = -AV_1 + \frac{1+A}{1+B} V_2}$$



Differentiator Amplifier

$$\frac{dy}{dx} / x''$$

R

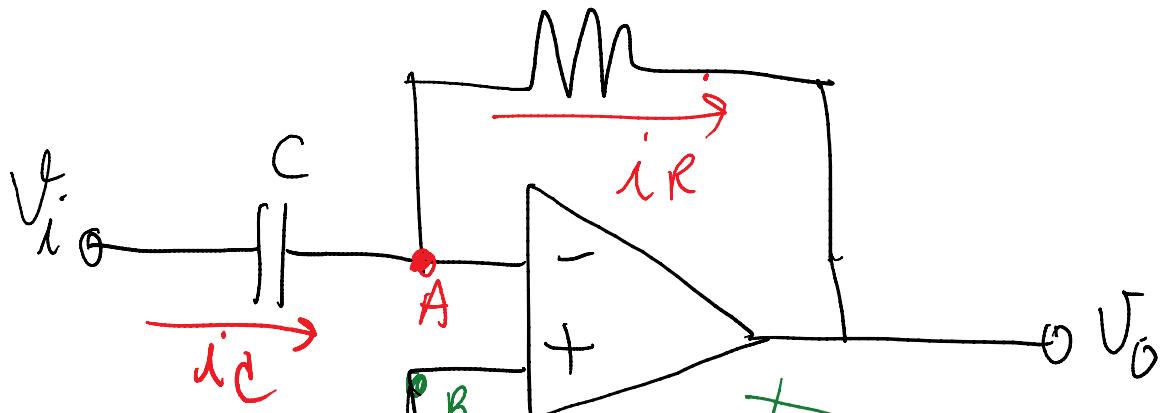

At node A $\frac{1}{j\omega} \frac{1}{LC} = j\omega k_c L$

$$i_C = C \frac{dV}{dt}$$

$$(V_i - V_A) S_C = \frac{V_A - V_0}{R}$$


$$V_A = 0$$

$$V_i S_C = -\frac{V_0}{R}$$

$$\frac{CdV_i}{dt} = -\frac{V_0}{R}$$

$$\frac{dV_i}{dt} = -\frac{1}{RC} \cdot V_0$$

Integrating Amplifier

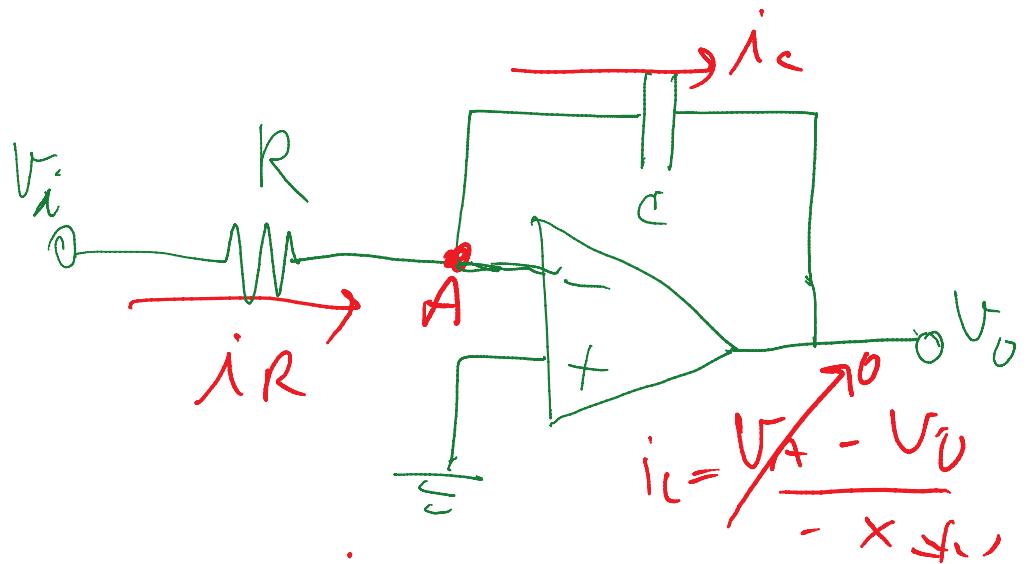

$$\therefore i_R = i_C$$

$$\frac{V_i}{R} = -C \frac{dV_o}{dt}$$

$$V_o = -\frac{1}{RC} \int V_i dt$$